



ECE316 Assignment 2

Full 4-bit Adder

Assignment 2. Full 4-bit Adder

Goal of this assignment:

- Be familiar with concurrent **port map** mechanism in VHDL
- Know how to use component defined in another file

Concurrent Statements	Sequential Statement
Assignment (arithmetic and logic)	Assignment (arithmetic and logic)
When ... else	If ... else
With ... Select	Case
Port map	While....Loop
	For ... Loop



How to Use VHDL Describe Hardware Dataflow

- Dataflow
 - The data flow describes how data moves through the circuit.
 - VHDL describes data flow using **concurrent signal assignment (port map)**
 - Each **concurrent statement** is **triggered** by **changes** on its inputs and delivers its outputs
 - There is no correspondence between the order of assignments in the source code.(pay attention to conflict)




Unsigned 4-bit Adder Function Specification

- Unsigned Full 4-bit Adder (4-bit Adder) adds two 4-bit binary numbers plus **Carry-on** input and gives 4-bit **SUM** and a **Carry-on** output.
- The Main operation of this 4-bit adder is to ripple each carry output to carry input of next single bit addition.
- Each single bit addition is performed with full 1-bit Adder operation (A, B, Cin) input and (Sum, Cout) output.
- The 4-bit Adder VHDL Code can be Easily Constructed by **Port Mapping** 4 1-bit Full Adder.


Concurrent Statements:

Port map Example:

- 4-bit full adder

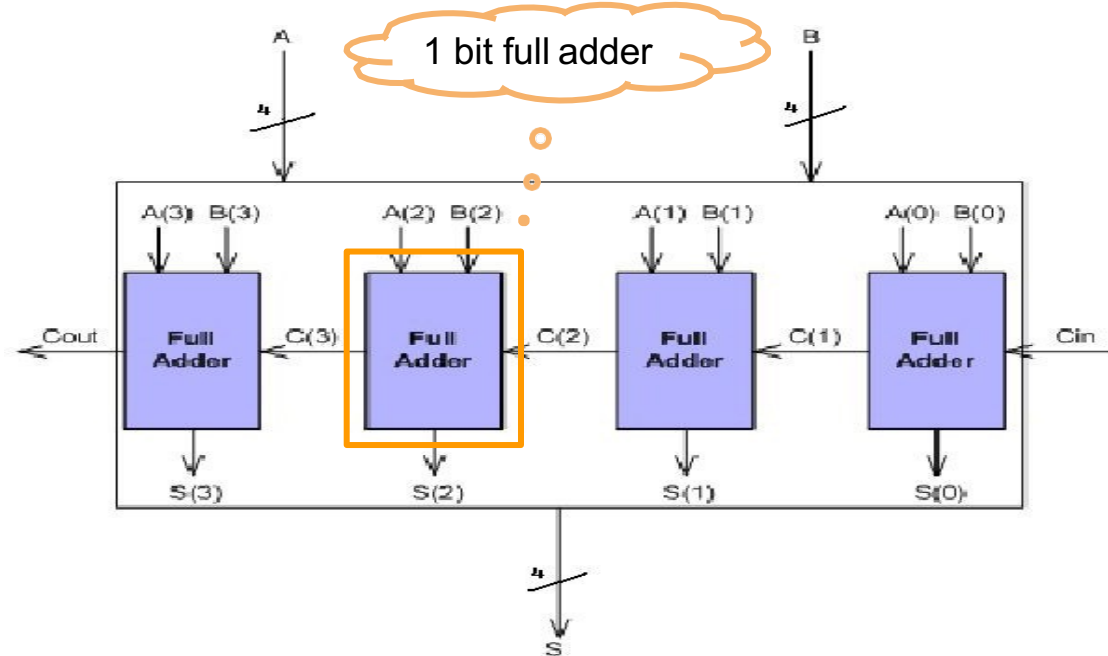

Full 4-bit adder

 


VHDL Operators

Class						
1. Logical operators	<code>and</code>	<code>or</code>	<code>nand</code>	<code>nor</code>	<code>xor</code>	<code>xnor</code>
2. Relational operators	<code>=</code>	<code>/=</code>	<code><</code>	<code><=</code>	<code>></code>	<code>>=</code>
3. Shift operators	<code>sll</code>	<code>srl</code>	<code>sla</code>	<code>sra</code>	<code>rol</code>	<code>ror</code>
4. Addition operators	<code>+</code>	<code>-</code>	<code>&</code>			
5. Unary operators	<code>+</code>	<code>-</code>				
6. Multiplying op.	<code>*</code>	<code>/</code>	<code>mod</code>	<code>rem</code>		
7. Miscellaneous op.	<code>**</code>	<code>abs</code>	<code>not</code>			

[Functional block implementation of 1 bit full adder]

$$S = X \oplus Y \oplus C_{in}$$

$$C = XY + (X \oplus Y)C_{in}$$

 


1-bit Full Adder

Entity FullAdder **is**
 port (X, Y, Cin : in bit;
 Cout, Sum : out bit);
End Full Adder;

Architecture behav **of** FullAdder **is**
begin

-----Please fill in this part-----

End behav;

 

[Concurrent Statements: Port map]

```
port map (signal1, signal2,...signaln);
```

```
instance_name : component name
```

```
    port map (port1=>signal1, port2=> signal2,... port3=>signaln);
```

- Describe sub-components of the circuit using VHDL program
- Describe interconnections between sub-components of the circuit using **Port Map** statement.

Interface Specification

Name	Bit Length	Mode	Description
A	4	Input	A operand
B	4	Input	B operand
Cin	1	Input	Carry-on Input
Sum	4	Output	Sum of A and B
Cout	1	Output	Carry-on Output

The 4-bit Ripple-Carry Full Adder (Unsigned)

Entity Adder4 is

port (A, B : in bit_vector (3 downto 0);
Cin : in bit;
S : out bit_vector (3 downto 0)
Cout : out bit);

End Adder4;

Architecture struct of Adder4 is

Component FullAdder

port (X, Y, Cin : in bit;
Cout, Sum : out bit);

End component;


Signal C : bit_vector(3 downto 1);

Begin

FA0 : FullAdder **port map** (A(0), B(0), Cin, C(1), S(0));

.....Fill In.....

End struct;

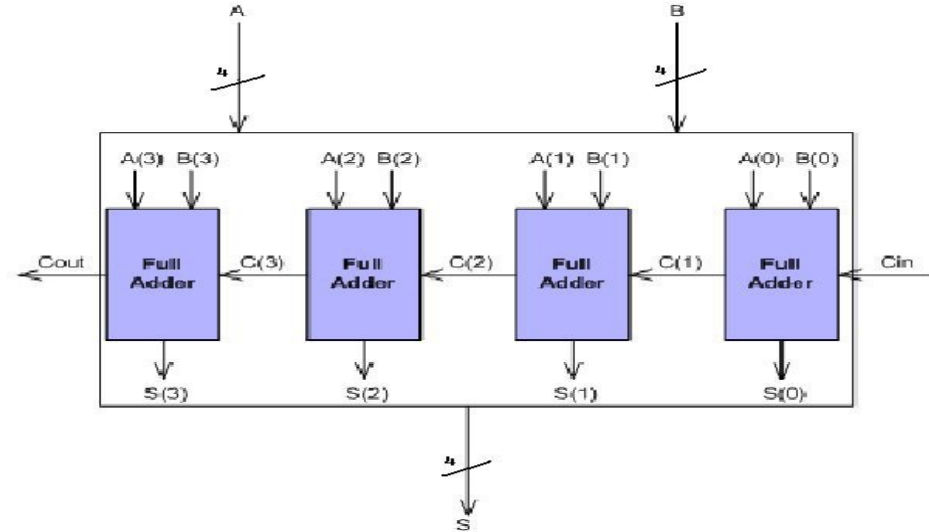

Simulation Example:

A = 1 1 1 1 (Unsigned)

B = 0 0 0 1 (Unsigned)

Cin = 0

Sum = 0 0 0 1

Cout = 1

Note: If A and B are both signed number, they do not have carry bit (Cout/Cin). For signed addition, it only has overflow bit. Also, for signed number, we always use the Most Significant Bit (MSB) to represent the sign.

Ripple-Carry Performance

Performance:

If each adder takes 5ns to calculate its output:

=> 5ns : C(1) and S(0)


=> 10ns : C(2) and S(1)

=> 15ns : C(3) and S(2)

=> 20ns : Cout and S(3)

Can show in simulation by adding a transport delay in the code:

A <= transport B after 5ns;

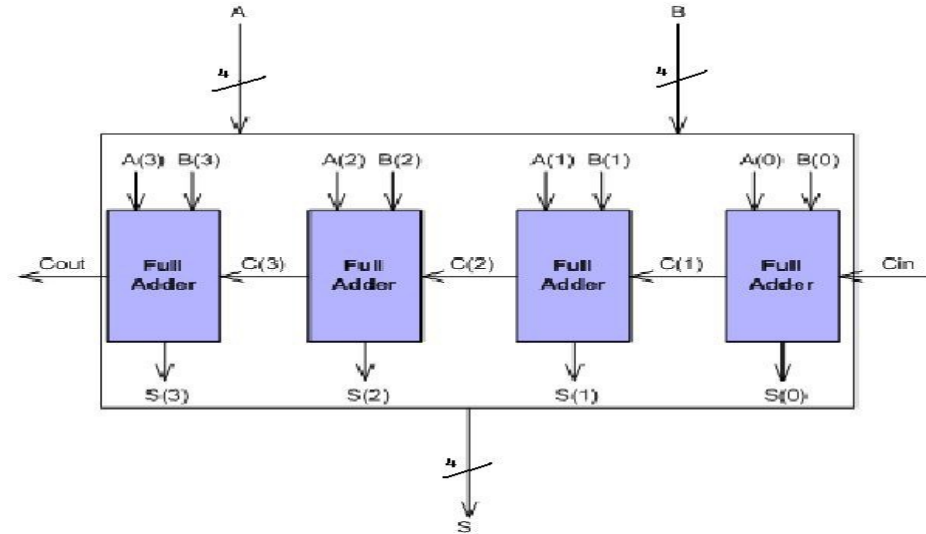

Carry Look Ahead Adder

To combat this, we can calculate the all the carries at the same time:

$$S_i = A_i \oplus B_i \oplus C_i$$
$$C_{i+1} = A_i B_i + (A_i + B_i) C_i$$

the carry logic can be separated into:

Generation:

$$G_i = A_i B_i$$

Propagation:

$$P_i = A_i + B_i$$

So:

$$C_{i+1} = G_i + P_i C_i$$

So we can then calculate the carry values for a 4-bit adder as

$$C_1 = G_0 + P_0 C_{in}$$

$$C_2 = G_1 + P_1 C_1$$

$$C_3 = G_2 + P_2 C_2$$

$$C_4 = G_3 + P_3 C_3$$

Carry Look Ahead Adder

By substituting the values of C:

$$C_1 = G_0 + P_0 C_{in}$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_{in}$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{in}$$

$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_{in}$$

Where:

$$G_i = A_i B_i$$

$$P_i = A_i + B_i$$

Partial 1-bit Full Adder with G and P

Name	Bit Length	Mode	Description
A	1	Input	A bit
B	1	Input	B bit
Cin	1	Input	Carry-in bit
Sum	1	Output	Sum of A and B
P	1	Output	A or B
G	1	Output	A and B


Carry Look Ahead Logic

Name	Bit Length	Mode	Description
P	4	Input	Propagaters
G	4	Input	Generators
Cin	1	Input	Carry-in bit
Cs	4	Output	Carry values

Interface Specification

Name	Bit Length	Mode	Description
A	4	Input	A operand
B	4	Input	B operand
Cin	1	Input	Carry-on Input
Sum	4	Output	Sum of A and B
Cout	1	Output	Carry-on Output

4-bit CLA Adder - Structure

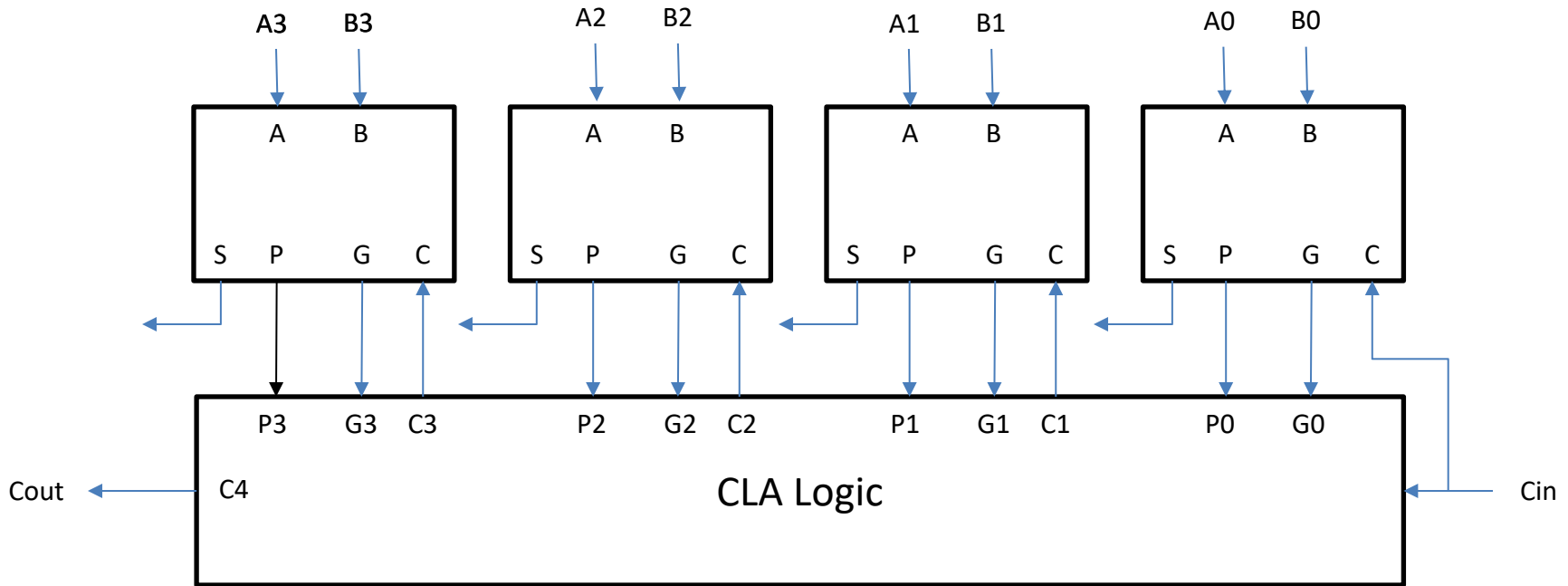

[Assignment 2 Due Date]

ModelSim Simulation Result + Lab Report
Deadline: Next class day (Blackboard submission)