
Building State Machines

The slide features decorative horizontal lines: a thick teal line at the top, a thin teal line below it, and another thick teal line at the bottom. Two short, thick olive-green dashes are positioned horizontally in the lower-middle section of the slide.

Two Types of Circuits in Digital System



Combinational logic circuits: The outputs depend solely on the inputs.

Assignment 3 Calculator

Sequential logic circuits: The outputs (next state) depend not only on the inputs, but also on the present state of system.

Project 1 FSM

Key features of a system can be modeled as FSM

- A state machine is a digital device that traverses through a **predetermined** sequence of states in an orderly fashion.
- The system can be described by a **finite** set of states.
- The system has a finite set of inputs and/or events that can **trigger transitions** between states.
- For each state the system may be in, the behavior is defined for **each possible input or event**.
- The system has a particular **initial state (reset states)**.

Two Types of State machine

 


Figure 1: Mealy Type Machine

Mealy machine: Output values are determined both by its **current state and the current inputs**

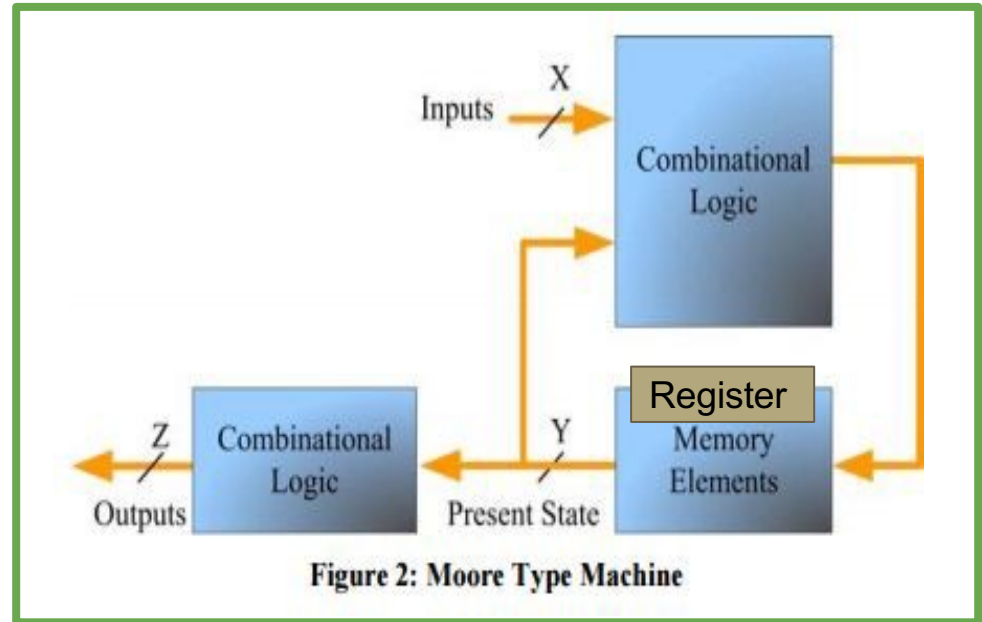


Figure 2: Moore Type Machine


Moore machine: Output values are determined **solely by its current state**

Project 1. Sequence Detector using FSM

Example: Detect Input Sequence


1101

(Overlap is allowed)

 

Input:	1	0	1	1	0	1	1	0	1	0	0	1	1	0	1	0
Output:	0	0	0	0	0	1	0	0	1	0	0	0	0	0	1	0

VHDL Moore Machine Block Diagram

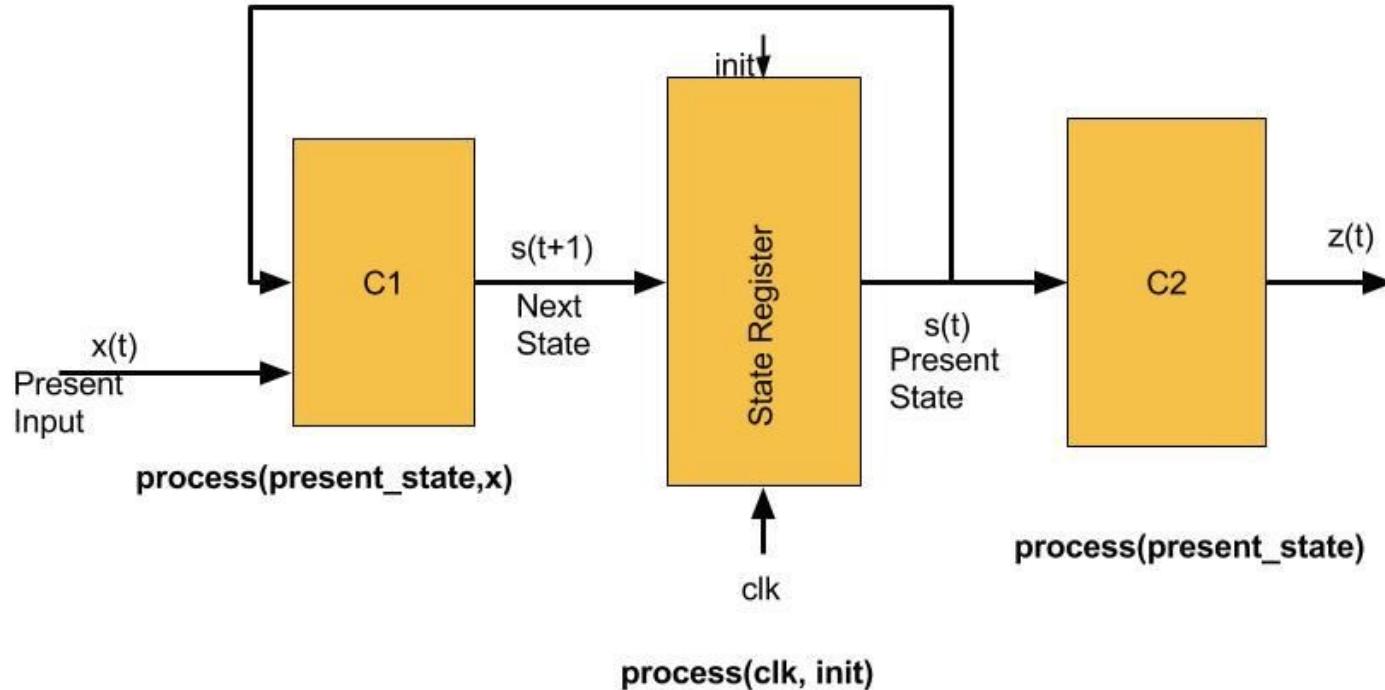

Moore Machine:
The output $z(t)$
only depends on
present state

Moore Machine Top Level

Interface Specification



--sequence detector

Library IEEE;

Use IEEE.STD_LOGIC_1164.**all**;

Entity fsm is

Port (clk: **in** STD_LOGIC;

init: **in** STD_LOGIC;

Din: **in** STD_LOGIC;

Dout: **out**

STD_LOGIC);


end fsm;

Architecture fsm of fsm is

type state_type **is** (s0, s1, s2, s3, s4);

Signal next_state, present_state: state_type;

begin

 

Sreg: **process** (clk, init)

Begin

If init = '1' **then**


present_state <= s0;

Elsif clk'event **and** clk='1' **then**

Present_state <= next_state;

end if;

End process;

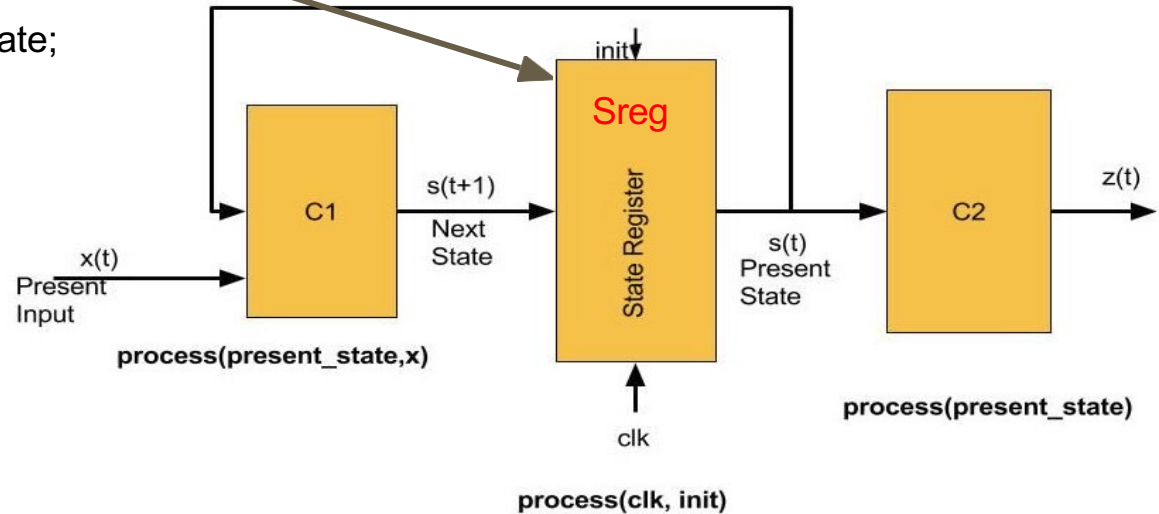

C1: **process** (present_state, din)

Begin:

Case present_state **is**

When s0 =>

If din = '1' **then**

Next_state <= s1;

Else

Next_state <= s0;

End if;

When s1=>


If din = '1' **then**


Next_state <= s2;

Else

Next_state <= s0;

End if;

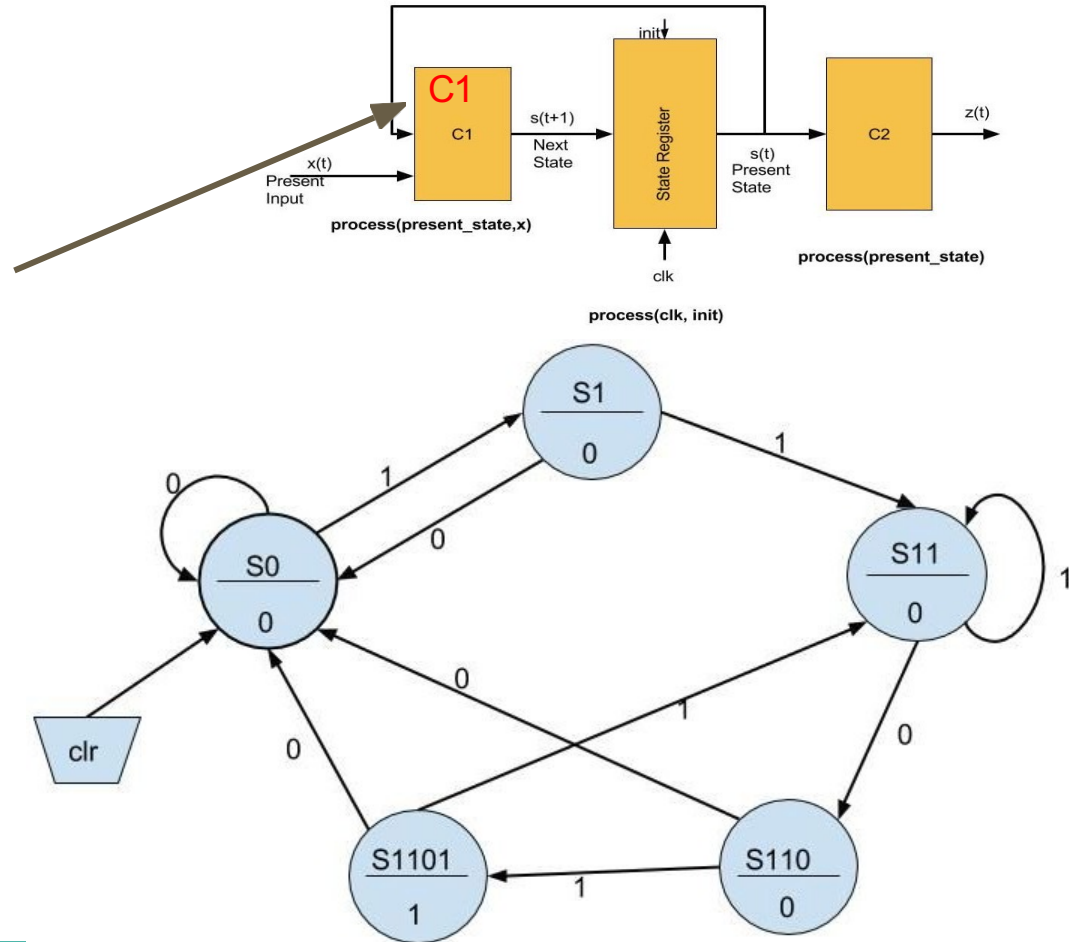


 

continue...

```

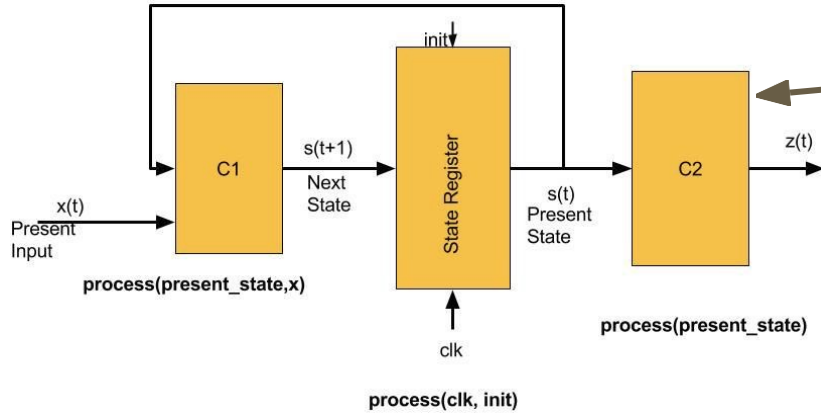When s2 =>
  If din = '0' then
    Next_state <= s3;
  Else
    Next_state <= s2;
  End if;
When s3 =>
  If din = '1' then
    Next_state <= s4;
  Else
    Next_state <= s0;
  End if;
When s4 =>
  If din='0' then
    Next_state <= s0;
  Else
    next_state<= s2;
  End if;
When others =>
  Null;
End case;
End process;
  
```



C2: **process**(present_state)

Begin

If present_state = s4 then
Dout <= '1';

Else

Dout <= '0';

End if;

End process;

End seqdata;


DE1 Board download

Clk : Key (Pulse)

Din : Toggle Switch

Init : Go back to the
initial state

Correct_Out: Green Led

 

Clock Division

The frequency divider is a simple component which objective is to **reduce the input frequency**. The component is implemented through the use of the ***scaling factor*** and a ***counter***. The ***scaling factor*** is the relation between the input frequency and the desired output frequency:

$$\text{Scale} = \frac{50\text{MHz}}{100\text{Hz}} = 500000$$

The ***counter*** is an n-bit counter will start counting the number of clock pulses.

Output Clock Frequency	Scale
50M Hz	1
1M Hz	50
1 Hz	50,000,000

Example of 3 bit Binary Counter

Clock Pulse	1st bit (MSB)	2nd	3rd (LSB)
0	0	0	0 (initial state)
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

Remain in State

- As you can see, if you use 2nd bit of output of counter as a clock input to another source, the frequency provided is essentially half of original frequency, while it is 1/4th of the original frequency if we use the 1st bit as output!
- After clock division, if we generate a 6 Hz clock to drive this state diagram then a delay of 1 second is achieved by staying in a state for 6 clock cycles. Similarly, a delay of 5 second is achieved by staying in a state for 30 ($6 * 5$) clock cycles. The counter variable in the state diagram will be reset to zero when moving to the next state after a timeout.

