

# ECE 316 – HW#3 - A

Simple ALU  
with  
Hardware Implementation

# Objective

- 8-bit **signed** adder
  - X, Y (1 bit sign, 7 bit value)
- Multiple operations


X (+0)	(0) - Y
X + 1	X + Y
X - 1	X - Y
(0) - X	Y - X

- Binary input
- Decimal Output

# SimpleALU – Inputs/Outputs

Pin/Bus	I/O	Size	Name
Din	Input	8-bits	Data load inputs
LoadX	Input	1-bit	Load X Register (active LOW)
LoadY	Input	1-bit	Load Y Register (active LOW)
Opr	Input	3-bits	Operation
Clk	Input	1-bit	Register Clock (Pulse, Falling Edge)
Dout0	Output	7-bits	7-segment Low Order digit
Dout1	Output	7-bits	7-segment High Order digit
Negative	Output	1-bit	Segment 6 on 7-segment display
Overflow	Output	1-bit	Overflow flag

# SimpleALU – External View

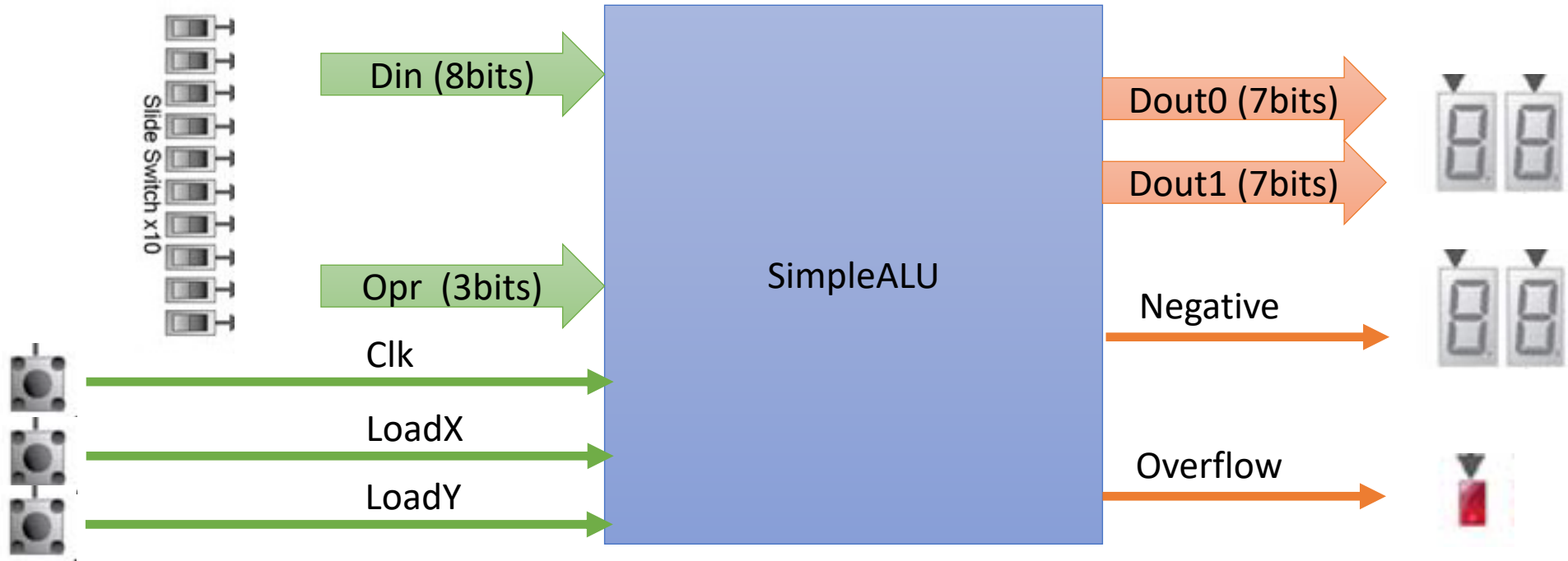

# SimpleALU - Operations


LoadX LoadY	Operation
11	Disable Load (default)
01	Load Register X
10	Load Register Y
00	Load X and Y

Opr	Operation/Output
0000	X (+0)
0001	X + 1
0010	X - 1
0011	-X
0100	-Y
0101	X + Y
0110	X - Y
0111	Y - X


## Constraints:

- X, Y are in range -99 to 99
- Results are range -99 to 99
- Overflow if outside range
- negative as 2's complement
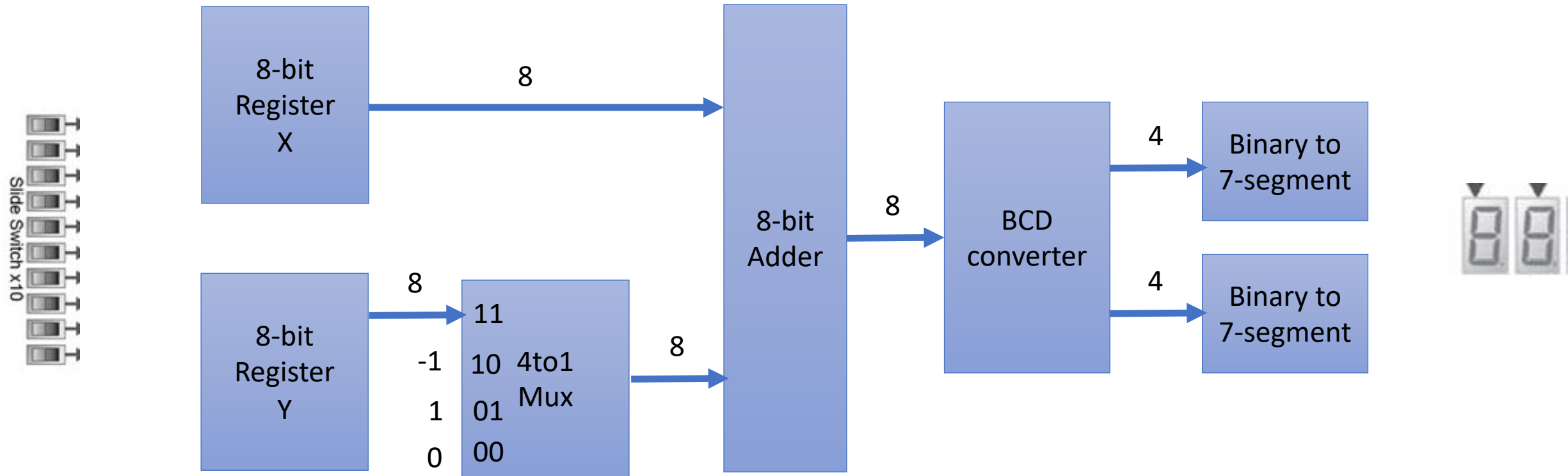
# Structural Design – from 3A – NOT VALID



# Structural Design – from 3B – Ver 1.

 

# Process Statement

Process (sensitivity-list)

--declaration

begin

--sequential statements

end process;

- Sensitivity list is a list of signals
- Any signal change inside sensitivity list will cause the process to execute
- Process itself is a concurrent statement

It is not allowed to use concurrent statements inside a process



# Sensitivity List Example

```
process (input_1, input_2)
```

```
begin
```

```
    and_gate <= input_1 and input_2;
```

```
end
```

```
Process;
```

- A change on either input\_1 or input\_2 will cause the Process to execute

# [ Sequential Statements ]

Concurrent Statements	Sequential Statement
Assignment ( arithmetic and logic)	Assignment ( arithmetic and logic)
When ... else	If ... else
With	Case
Port map	While ... loop
	For ... loop

# Sequential Statements:

## if ... else

```
if condition then  
    sequential statements  
    [elsif condition then  
        sequential statements ]  
    [else  
        sequential statements ]  
end if;
```

# Sequential Statements: case

```
case expression is
  when choices =>
    sequential statements
  when choices =>
    sequential statements
    -- branches are allowed
  [ when others => sequential statements ]
end case;
```

# Sequential Statements: for ... loop

```
[ loop_label :] for identifier in range loop  
    sequential statements  
    [next   [label] [when condition];  
    [exit   [label] [when condition];  
end loop[ loop_label ];
```

# Sequential Statements:

## while ... loop

```
[ loop_label :] while condition loop  
    sequential statements  
    [next   [label] [when condition];  
    [exit   [label] [when condition];  
end loop[ loop_label ];
```

```
Library IEEE;  
Use IEEE.std_logic_1164.all;
```

```
Entity xor_sig is
```

```
Port (  
A, B,C: in STD_LOGIC;  
X,Y: out STD_LOGIC  
);  
End xor_sig
```

```
Architecture SIG_ARCH of xor_sig is  
Signal D: STD_LOGIC;  
Signal E: STD_LOGIC;  
Signal F: STD_LOGIC;
```

```
Begin
```

```
Process(A,B,C)
```

```
Begin
```

```
    D <= A;           -- ignored  
    E <= D xor F; --OLD value of D  
    F <= B xor D; --OLD value of D  
    X <= C xor E; --OLD value of E  
    D <= B;           --D's value gets overwritten  
                    by B after process ends  
    Y <= D xor F; --OLD value of D and F
```

```
End process
```

```
End SIG_ARCH
```

```
Library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_unsigned.all;
```

```
Entity xor_var is
```

```
Port (  
A, B,C: in STD_LOGIC;  
X,Y: out STD_LOGIC  
);  
End xor_var
```

```
Architecture VAR_ARCH of xor_var is  
variable D: STD_LOGIC;  
variable E: STD_LOGIC;  
variable F: STD_LOGIC;  
variable P: STD_LOGIC;  
variable Q: STD_LOGIC;
```

```
Begin
```

```
Process(A,B,C)
```

```
Begin
```

```
    D := A;           --D is assigned with value of A  
    E := D xor F; --New value of D (A)  
    F := B xor D; --New value of D (A)  
    X := C xor E; --New value of E  
    D := B;           --D value is changed to B  
    Y := D xor F; --New value of both D and F
```


```
    X <= P
```

```
    Y <= Q
```

```
End process
```

```
End VAR_ARCH
```

# SimpleALU – Internals – disp7

 

## **Operation:**

Seven segment display logic

Converts 4-bit binary input to decimal value:


0,1,2,3,4,5,6,7,8,9

7-bits refer to segments 0-6 on display



# 7 Segment Display Patterns and Truth Table (ECE315)

	<i>Input</i> X3..X0	<i>Display</i> D6 ... D0
0	0 0 0 0	1 0 0 0 0 0 0
1	0 0 0 1	
2	0 0 1 0	
3	0 0 1 1	
4	0 1 0 0	
5	0 1 0 1	
6	0 1 1 0	
7	0 1 1 1	
8	1 0 0 0	
9	1 0 0 1	
10	1 0 1 0	X X X X X X X X
11	1 0 1 1	X X X X X X X X
12	1 1 0 0	X X X X X X X X
13	1 1 0 1	X X X X X X X X
14	1 1 1 0	X X X X X X X X
15	1 1 1 1	X X X X X X X X

 

The 7 segment displays on DE1 board are designed to light up when applying a low level voltage.

Applying a Vcc to display will turn off the LEDs.

# K-Map (ECE315)


- We have 4 inputs and 7 outputs.
- Implement in VHDL as equations

	<i>Input</i> X3..X0	<i>Display</i> D6...D0
0	0 0 0 0	1 0 0 0 0 0 0
1	0 0 0 1	
2	0 0 1 0	
3	0 0 1 1	
4	0 1 0 0	
5	0 1 0 1	
6	0 1 1 0	
7	0 1 1 1	
8	1 0 0 0	
9	1 0 0 1	
10	1 0 1 0	X X X X X X X X
11	1 0 1 1	X X X X X X X X
12	1 1 0 0	X X X X X X X X
13	1 1 0 1	X X X X X X X X
14	1 1 1 0	X X X X X X X X
15	1 1 1 1	X X X X X X X X

# 7-Segment Display Circuit - VHDL

- 1. Do K-maps and get minimal equations, implement with equations
- 2. Implement table directly in VHDL using:
  - Concurrent
    - When ... else
    - With ... select when
  - Process
    - If ... else
    - Case

# SimpleALU – Internals – BCDconv

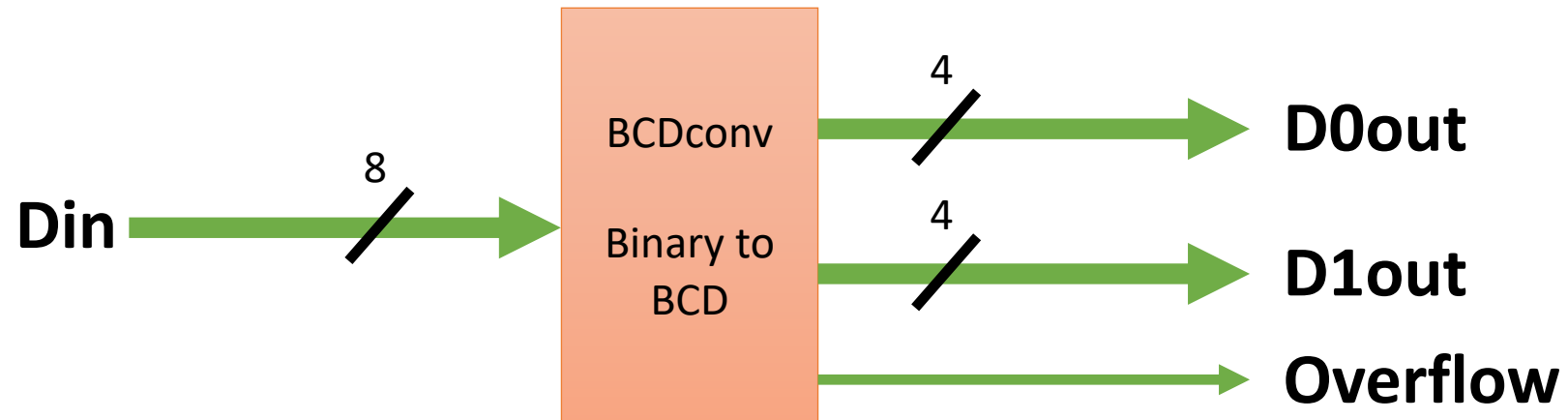

## Operation:

Converts a unsigned 8-bit binary number in the  
Range: 0 to +99  
to two decimal numbers with overflow

# Shift Add 3 Algorithm

- Do 8 times (for 8 bit binary input).
  - 1. Shift left one to the binary input.
  - 2. Add 3 to BCD if it's greater than 4.
  - 3. Go to 1.

# Shift Add 3 Algorithm (ECE315)

- Input = HGFE DCBA
- Take the first 3 MSB of inputs and add to output.
  - Output = 0000 0HGF
- If  $00HGF > 4$ 
  - $I\ H1\ G1\ F1 = 0\ H\ G\ F + 0011.$
- Else
  - $I\ H1G1F1 = 0\ H\ G\ F$
- Shift left one.
  - Output = 000I H1 G1 F1 E
- If  $H1\ G1\ F1\ E > 4$ 
  - $H2\ G2\ F2\ E1 = H1\ G1\ F1\ E + 0011.$
- Else
  - $H2\ G2\ F2\ E1 = H1\ G1\ F1\ E$
- Shift left one.
  - Output = 00I H2 G2 F2 E1 D
- If  $G2\ F2\ E1\ D > 4$ 
  - $G3\ F3\ E2\ D1 = G2\ F2\ E1\ D + 0011.$
- Else
  - $G3\ F3\ E2\ D1 = G2\ F2\ E1\ D$
- Shift left one.
  - Output = 0I H2 G3 F3 E2 D1 C
- If  $0I\ H2\ G3 > 4$ 
  - $J\ I1\ H3\ G4 = 0\ I\ H2\ G3 + 0011.$
- Else
  - $J\ I1\ H3\ G4 = 0\ I\ H2\ G3$
- If  $F3\ E2\ D1\ C > 4$ 
  - $F4\ E3\ D2\ C1 = F3\ E2\ D1\ C + 0011.$
- Else
  - $F4\ E3\ D2\ C1 = F3\ E2\ D1\ C$
- Shift left one.
  - Output = I1 H3 G4 F4 E3 D2 C1 B
- If  $I1\ H3\ G4\ F4 > 4$ 
  - $I2\ H4\ G5\ F5 = I1\ H3\ G4\ F4 + 0011.$
- Else
  - $I2\ H4\ G5\ F5 = I1\ H3\ G4\ F4$
- If  $E3\ D2\ C1\ B > 4$ 
  - $E4\ D3\ C2\ B1 = E3\ D2\ C1\ B + 0011.$
- Else
  - $E4\ D3\ C2\ B1 = E3\ D2\ C1\ B$
- Shift left one.
  - Output = H4 G5 F5 E4 D2 C2 B1 A

# Add 3 Circuit (ECE315)

- If Input  $> 4$
- Output = Input + 3;
- Else
- Output = Input;
- End

Input = 0101 (which is greater than 4)  
Output = 0101 + 0011 = 1000

Input X3X2X1X0	Output P3P2P1P0	
0000	0000	When <i>input</i> $\leq 4$ .
0001	0001	
0010	0010	
0011	0011	
0100	0100	
0101	1000	Fill these outputs
0110	1001	
0111		
1000		
1001		
1010	xxxx	When input $> 9$ , don't care.
.	.	
.	.	
1111	xxxx	


# Add-3 Circuit

- 1. Do K-maps and get minimal equations, implement with equations
- 2. Implement table directly in VHDL using:
  - Concurrent
    - When ... else
    - With ... select when
  - Process
    - If ... else
    - Case
- 3. Implement as arithmetic
  - variable bcddigit : std\_logic\_vector(3 downto 0);
  - bcddigit := std\_logic\_vector(unsigned(bcddigit) + "0011");
    - use ieee.numeric\_std.all;



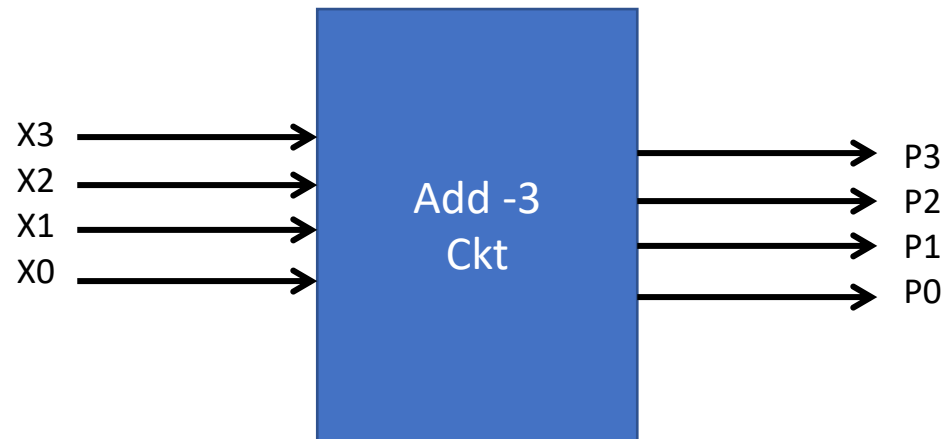
# Add 3 Circuit (ECE315)


- Complete the Truth Table from prev slide
- Find the Boolean expression for P3, P2, P1 and P0.
- Implement in VHDL



- If  $0HGF > 4$ 
  - $I\ H1\ G1\ F1 = 0\ H\ G\ F + 0011.$
- Else
  - $I\ H1G1F1 = 0\ H\ G\ F$
- Shift left one.
  - **Output = 000I H1 G1 F1 E**
- If  $H1\ G1\ F1\ E > 4$ 
  - $H2\ G2\ F2\ E1 = H1\ G1\ F1\ E + 0011.$
- Else
  - $H2\ G2\ F2\ E1 = H1\ G1\ F1\ E$
- Shift left one.
  - **Output = 00I H2 G2 F2 E1 D**
- If  $G2\ F2\ E1\ D > 4$ 
  - $G3\ F3\ E2\ D1 = G2\ F2\ E1\ D + 0011.$
- Else
  - $G3\ F3\ E2\ D1 = G2\ F2\ E1\ D$
- Shift left one.
  - **Output = 0I H2 G3 F3 E2 D1 C**
- If  $0I\ H2\ G3 > 4$ 
  - $J\ I1\ H3\ G4 = 0\ I\ H2\ G3 + 0011.$
- Else
  - $J\ I1\ H3\ G4 = 0\ I\ H2\ G3$
- If  $F3\ E2\ D1\ C > 4$ 
  - $F4\ E3\ D2\ C1 = F3\ E2\ D1\ C + 0011.$
- Else
  - $F4\ E3\ D2\ C1 = F3\ E2\ D1\ C$
- Shift left one.
  - **Output = I1 H3 G4 F4 E3 D2 C1 B**
- If  $I1\ H3\ G4\ F4 > 4$ 
  - $I2\ H4\ G5\ F5 = I1\ H3\ G4\ F4 + 0011.$
- Else
  - $I2\ H4\ G5\ F5 = I1\ H3\ G4\ F4$
- If  $E3\ D2\ C1\ B > 4$ 
  - $E4\ D3\ C2\ B1 = E3\ D2\ C1\ B + 0011.$
- Else
  - $E4\ D3\ C2\ B1 = E3\ D2\ C1\ B$
- Shift left one.
  - **Output= H4 G5 F5 E4 D2 C2 B1 A**
- **Let's the final output of BCD = U3U2U1U0 L3L2L1L0**

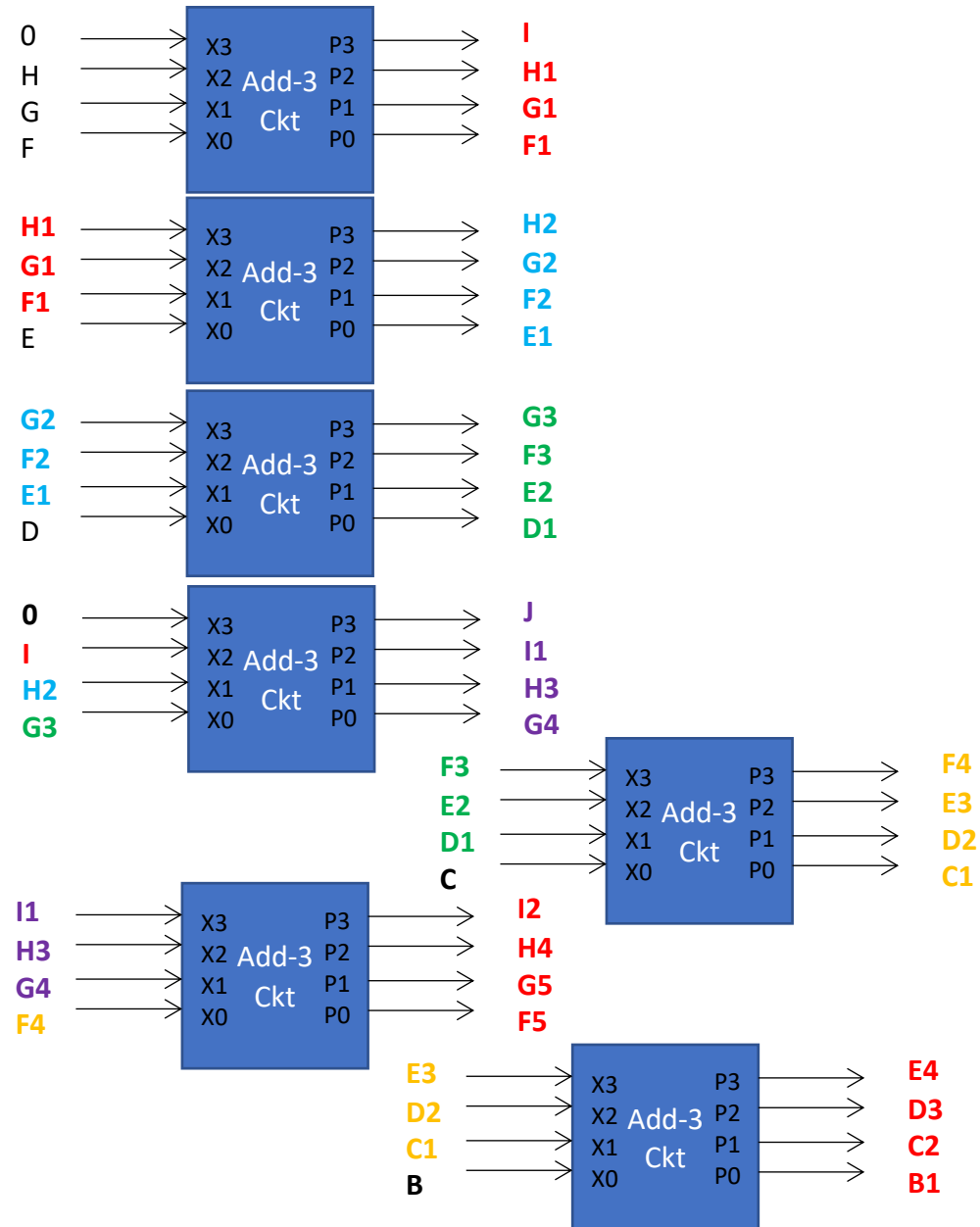

# BCD

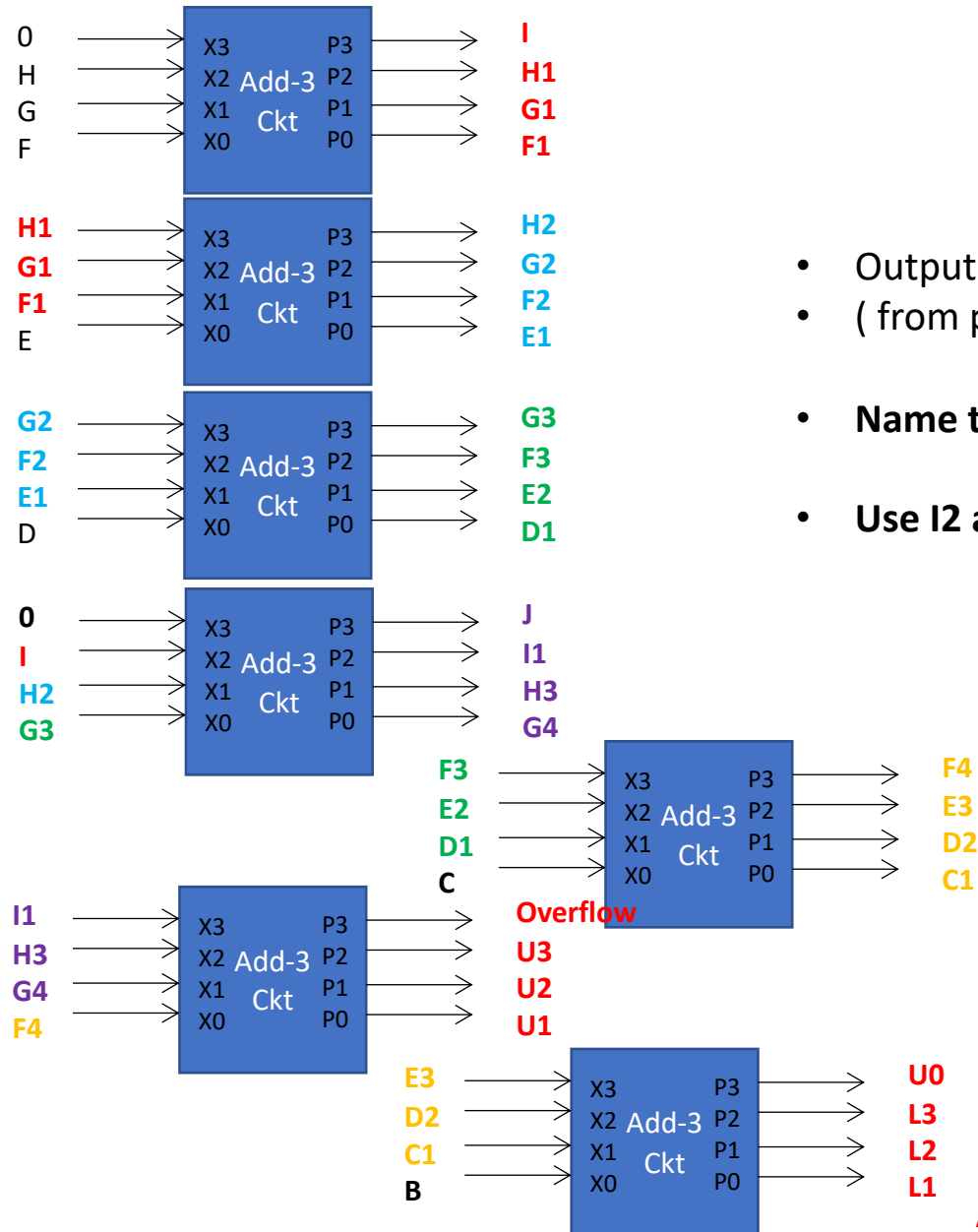


- Output= H4 G5 F5 E4 D3 C2 B1 A
- ( from previous slide)
- Name the final output of BCD as
  - Output = U3U2U1U0 L3L2L1L0
- Use I2 as Overflow.

A = L0.

# Shift-Add-3 Algorithm - VHDL

- Implement as a process using:
  - for loop
  - and if .. then statements
- Shift can be implemented as a concatenate
  - variable x : std\_logic\_vector(3 downto 0);
  - variable y : std\_logic\_vector(3 downto 0);
  - To left shift high-bit from x into y:
  - y := y(2 downto 0) & x(3);

# SimpleALU – Internals – addopr

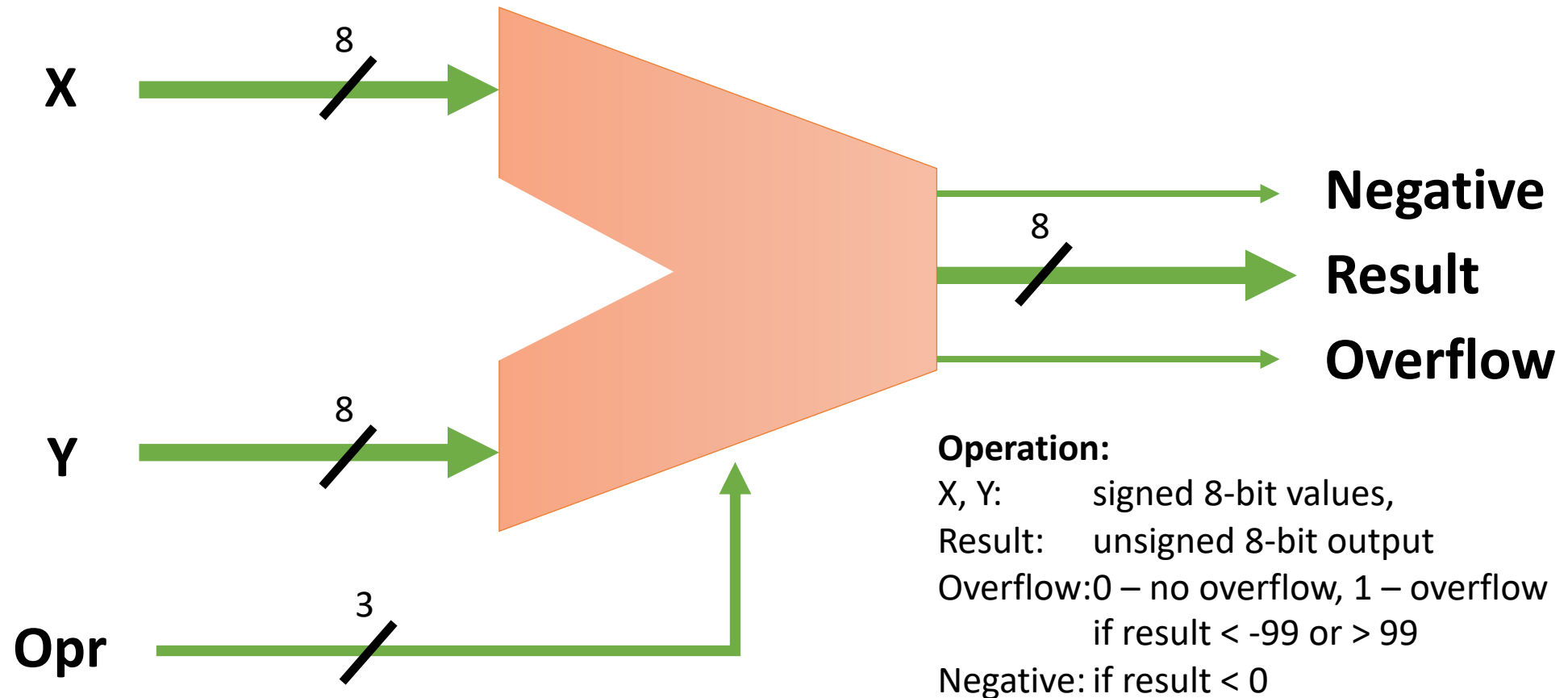


# Data Types

- bit {'0','1'}
- bit\_vector
- ieee.std\_logic:
  - std\_logic {'0', '1', 'Z', 'X'}
  - std\_logic\_vector
    - Range Declaration (e.g. 8 bits)
    - E.g. 7 downto 0, 8 downto 1
    - E.g. 0 to 7, 1 to 8

# Data Types

- `ieee.logic_signed`:
  - Signed integers
  - Operators (+, -, x, /)
    - Using signed arithmetic
- `ieee.numeric_std`:
  - Logic and arithmetic
  - Conversion functions

# SimpleALU – Internals – register8

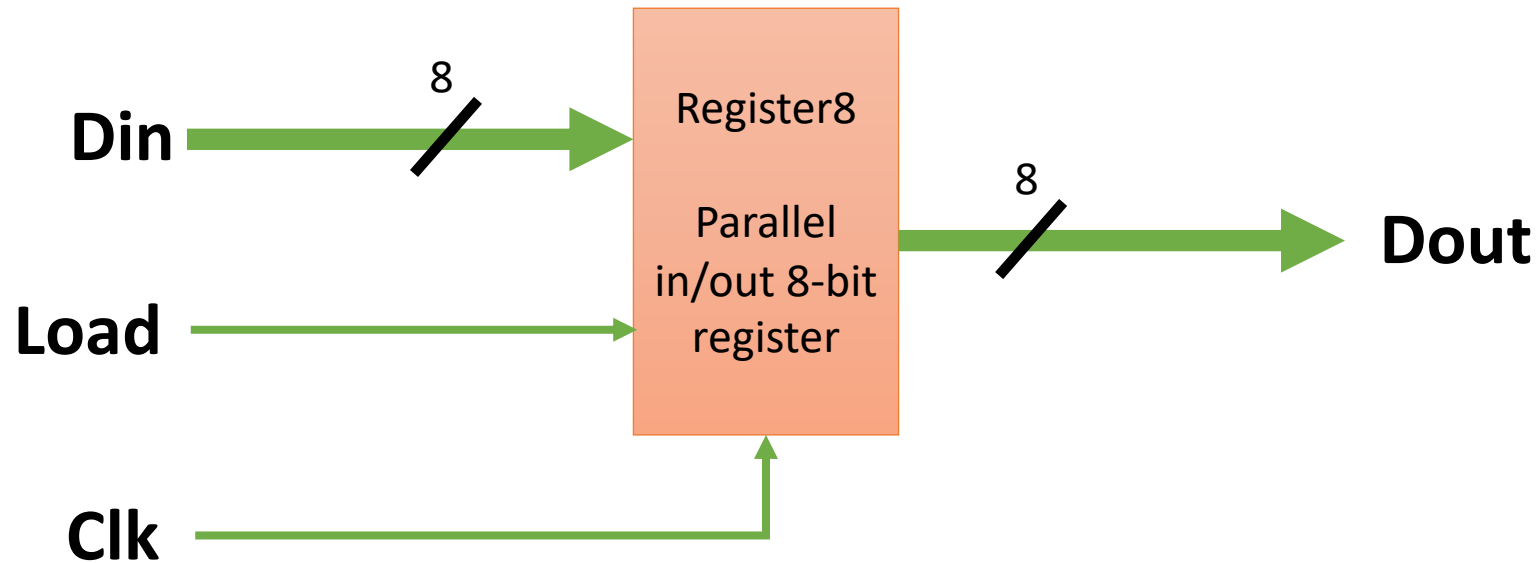

## Operation:

Load = 0:

Load Din to Internal on Clk falling edge  
Load internal to Dout on Clk rising edge

Load = 1:

Hold Dout, ignore Din




# Adjustments

- Load is active LOW
- Clock is active LOW

Din	Load	<i>Store</i>	Clk	Dout	Note
X	1	Store	X	Dout	Hold last value
X	0	Din	↓	Dout	Din to internal storage
X	0	Store	↑	Store	Internal storage to Dout

# Structural Design – from 3B – Ver 1.

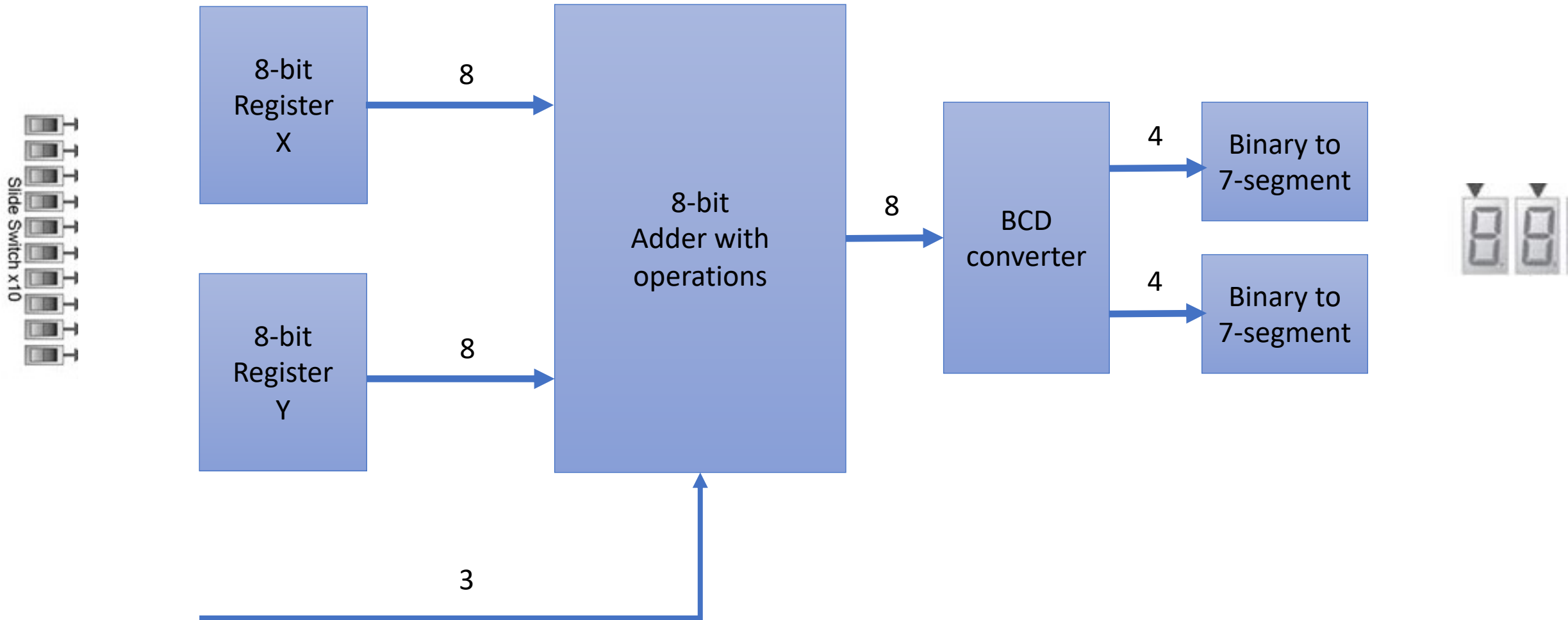

# To Demo – 3b

- Implement all components as VHDL
- Create a top-level design with these components
- Simulate in Modelsim (for report)
- Demo on DE1 board
  - Show all operations for at least 3 values of X and Y
  - Show the overflow
  - Show negatives